

SOLUTION TO THE EXPERIMENTAL COMPETITION

Galvanic cells

Part 1. Characteristics of the galvanic cell “Camelion”.

1.1 – 1.3 Table 1 shows the results of measuring resistances R_{0k} and voltages U_k , as well as the results of calculating currents I_k


Table 1

k	$R_{0k}, \text{ Ohm}$	$U_k, \text{ V}$	$I_k, \text{ A}$
1	1,0	1,300	1,300
2	2,0	1,405	0,703
3	3,0	1,445	0,482
4	4,0	1,470	0,368
5	5,0	1,480	0,296

Current strengths are calculated according to Ohm's law

$$I_k = \frac{U_k}{R_k}, \quad (1)$$

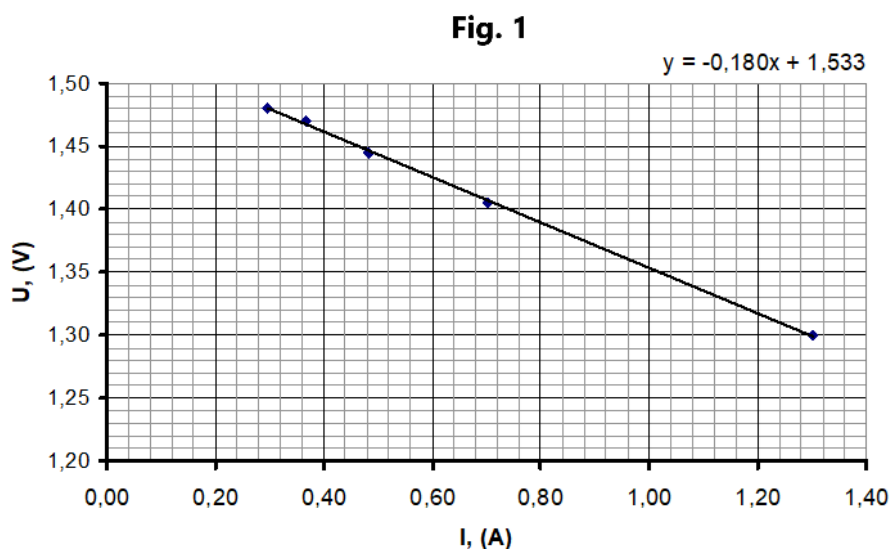and the graph of the obtained dependence is shown in Figure 1.



1.4 The theoretical dependence of the voltage in the external circuit on the current strength follows from Ohm's law:

$$U = \varepsilon - IR. \quad (2)$$

Using the least squares method, we find the parameters of the linear dependence $U = aI + b$. As follows from formula (2), the characteristics of the galvanic element are equal to:

$$\varepsilon = b = (1,53 \pm 0,04) \text{ V}, \quad (3)$$

$$r = -a = (0,18 \pm 0,02) \text{ Ohm}. \quad (4)$$

Part 2. Homemade galvanic cell.

2.1 The following circuit is used. A fixed resistor $R_0 = 10,0 \text{ kOhm}$ and a variable resistor of $20,0 \text{ kOhm}$ are used. The voltage U_0 was measured on the resistor R_0 , in which the current strength is calculated as:

$$I = \frac{U_0}{R_0}. \quad (5)$$

The voltage on the external circuit is also measured directly as U .

2.2 The measurement results are shown in Table 2 and in the graph in Fig. 2.


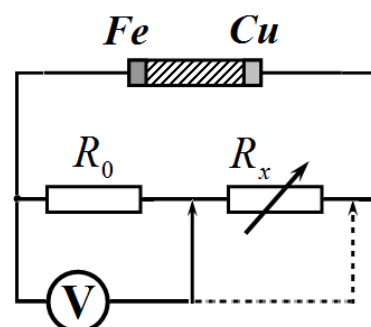


Table 2.

U_0 , mV	U , mV	I , mA
269	272	32,7
241	289	29,3
210	310	25,5
191	320	23,2
178	328	21,7
162	340	19,7
153	346	18,6
146	351	17,8
126	366	15,3
117	373	14,2
107	381	13,0

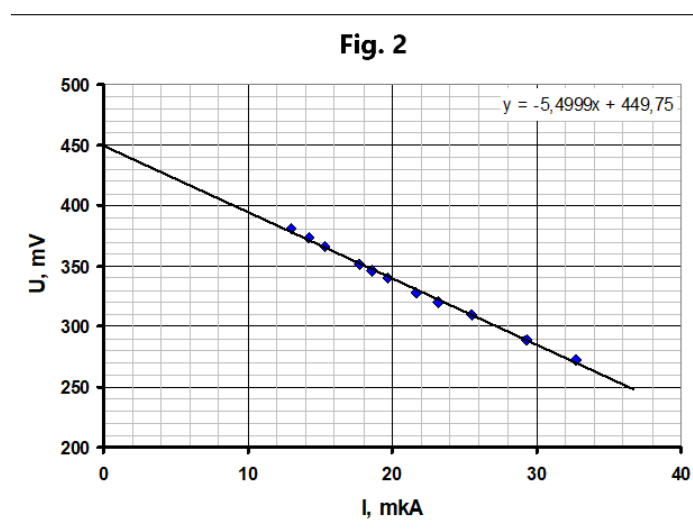

2.3 The calculation by the least squares method gives the following characteristics of a homemade cell

$$r = (5,5 \pm 0,5) \text{ k}\Omega, \quad (6)$$

$$\varepsilon = (450 \pm 13) \text{ mV}. \quad (7)$$

Part 3. Connections of galvanic cells.


3.1-3.2 When connected in series, the EMF is equal to the sum (approximately 2 V) or the difference (approximately 1 V) of the EMF of the sources. When connected in parallel, the total EMF is equal to the EMF of the industrial element, approximately 1.5 V (its resistance is lower).

Part 4. Current-voltage characteristic of a galvanic cell.

4.1 When using a source according to the variable resistor circuit, the following results are obtained, Table 3 and graph in Fig. 3.

Table 3.

«+» - «-»			«-» - «+»		
U_0 , mV	U , mV	I , mA	U_0 , mV	U , mV	I , mA
-722	793	-87,8	1003	-514	122,0
-665	777	-80,9	907	-483	110,3
-579	748	-70,4	829	-460	100,9
-528	731	-64,2	757	-431	92,1
-466	710	-56,7	715	-414	87,0
-409	687	-49,8	685	-403	83,3
-378	677	-46,0	620	-374	75,4
-352	669	-42,8	570	-350	69,3
-329	660	-40,0	521	-324	63,4
-279	642	-33,9	485	-274	59,0
-255	633	-31,0	463	-267	56,3
-251	631	-30,5	434	-236	52,8
			406	-191	49,4
			386	-153	47,0

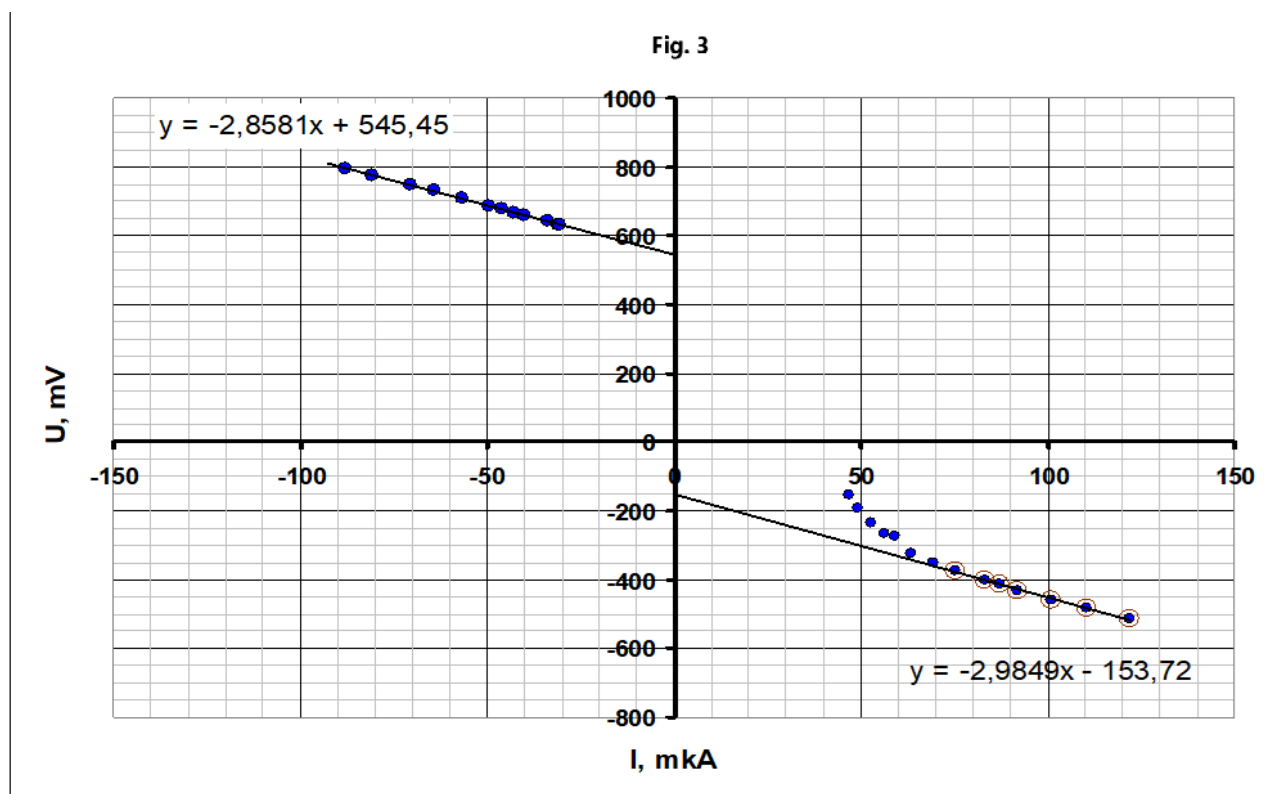

4.2 It is evident that when the direction of the current changes, the polarity of the galvanic cell changes.

Parameters of the linear dependence:

$$r = (2,9 \pm 0,2) \text{ kOhm}, \quad (8)$$

$$\varepsilon = (545 \pm 10) \text{ mV}, \quad (9)$$

which is close to the previously obtained values. However, these values still differ significantly, which is explained by the restructuring of double electric layers near the electrodes when current flows.

The second linear dependence is paradoxical, since the polarity of the element changes:

$$r = (3,0 \pm 0,4) \text{ kOhm}, \quad (10)$$


$$\varepsilon = -(154 \pm 42) \text{ mV}. \quad (11)$$

4.3 Using a source according to the potentiometer circuit expands the range of current variation in the circuit. The measurement results are presented in Table 4 and on the graph in Fig. 4

Table 4

«+» - «-»			«-» - «+»		
U_0 , mV	U , mV	I , mA	U_0 , mV	U , mV	I , mA
-733	790	-89,2	982	-541	119,5
-649	764	-79,0	908	-514	110,5
-619	755	-75,3	826	-483	100,5
-529	725	-64,4	716	-439	87,1
-489	712	-59,5	550	-269	66,9
-429	692	-52,2	477	-183	58,0
-374	673	-45,5	396	-6	48,2
-313	651	-38,1	349	103	42,5
-277	638	-33,7	296	217	36,0
-193	606	-23,5	261	261	31,8
-135	581	-16,4			
-69	548	-8,4			
-29	524	-3,5			
16	493	1,9			

48	471	5,8			
84	442	10,2			
124	414	15,1			
180	375	21,9			
252	326	30,7			
291	299	35,4			

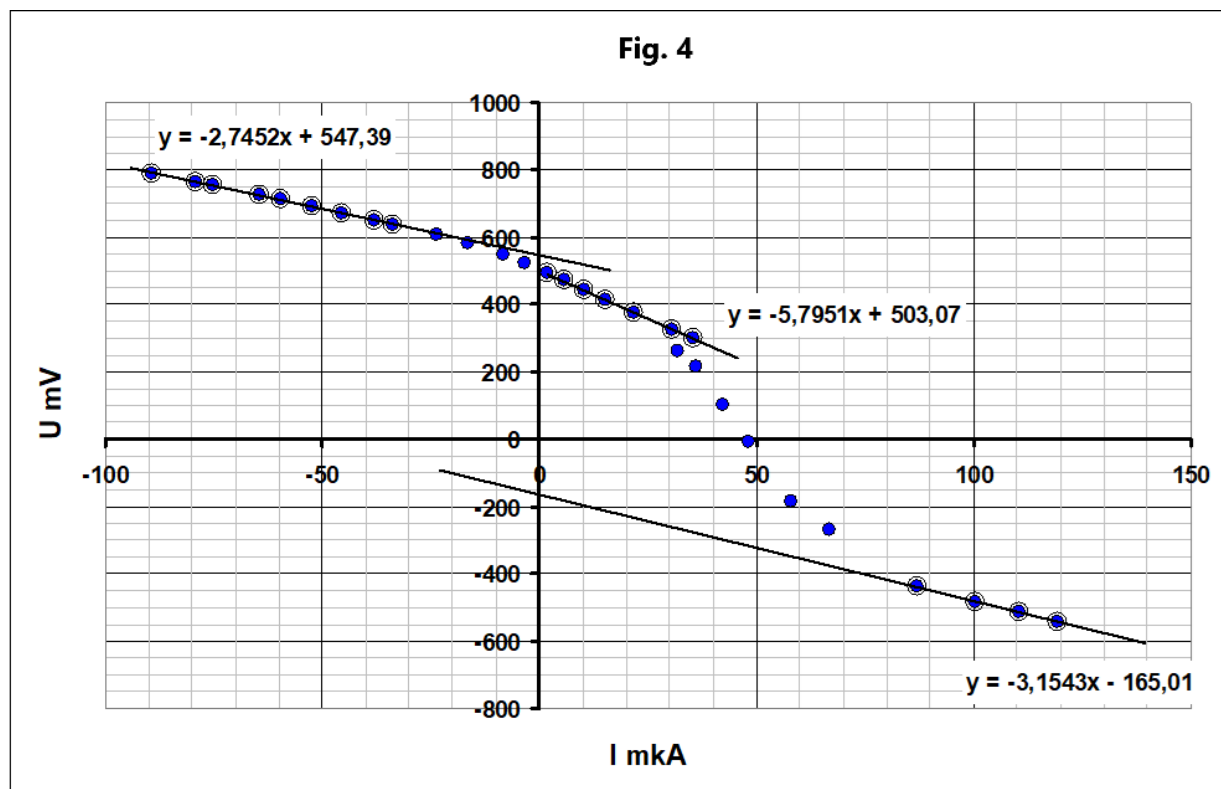

4.4 It turns out that repolarization occurs not at zero current, but at a current in the range of approximately 50 μA .

Three linear sections are distinguished (as the current increases), the values of EMF and internal resistance in these ranges are found as:

First section:

$$r = (2,75 \pm 0,14) \text{ k}\Omega, \quad (12)$$

$$\varepsilon = (547 \pm 5) \text{ mV}, \quad (13)$$

which coincides with the values obtained earlier.

Second section:

$$r = (5,80 \pm 0,24) \text{ k}\Omega, \quad (14)$$

$$\varepsilon = (503 \pm 5) \text{ mV}, \quad (15)$$

which clearly shows a change in the internal resistance of more than 2 times when the direction of the current changes.

Third section: (polarity reversal):

$$r = (3,15 \pm 0,14) \text{ k}\Omega, \quad (16)$$

$$\varepsilon = -(165 \pm 14) \text{ mV}, \quad (17)$$

which also almost coincides with the values obtained in section 4.1.

Grading scheme

If the dimension of the measured value is not specified, the result is not graded!

Part	Content	Total	Points
Part 1. Characteristics of the galvanic cell "Camelion".		3,0	
1.1	Resistance measurements $0,1 \times 5 = 0,5$	0,5	0,5

	allowable error $\pm 0,2$ Ohm		
1.2	Voltages are measured $0,1 \times 5 = 0,5$ allowable error $\pm 0,2$ V	0,5	0,5
1.3	Formula (1) Currents calculations (<i>only those points that are graded in parts 1.1 – 1.2</i>) $0,1 \times 5 = 0,5$ Graph: - axes are labeled and ticked; - all points are plotted in accordance with the table; - a smoothing straight line is drawn.	1,0	0,2 0,5 0,1 0,1 0,1
1.4	Theoretical dependence (3); Calculation of element characteristics using least squares method (<i>graphically by two points</i>); EMF value in the range $\epsilon 1,55 - 1,65$ V; ($1,40 - 1,70$ V); Internal resistance value in the range $0,1 - 0,3$ Ohm ($0,05 - 0,5$ Ohm) The error assessment of the parameters is carried out $2 \times 0,1$	1,0	0,1 0,3(0,2;0,1) 0,2 (0,1) 0,2(0,1) 0,2
Part 2. Homemade galvanic cell.		3,0	
2.1	Measurement circuit: a resistor, a variable resistor, and a galvanic cell are connected in series; 2 voltmeter connections; - a resistor of 10 kOhm is used; - a variable resistor of 20 kOhm is used; - two voltages are measured; - formula for the electric current: - the voltage on the external circuit is measured or calculated	1,0	0,4 0,1 0,1 0,2 0,1 0,1
parts 2.2 and 2.3 are graded, if the electric circuit has been graded!			
2.2	Measurements: - 8 number of points or more ($5 - 7$; <i>less than 5</i>); - the lower limit of the current strength is less than $200 \mu\text{A}$; - the upper limit of the current strength is more $1000 \mu\text{A}$. Graph (as in part 1.3): A linear decreasing dependence is obtained $U(I)$. <i>The inverse dependence is drawn $I(U)$ (-0,2 points)</i>	1,0	0,3(0,2;0,1) 0,1 0,1 0,3 0,2
2.3	Element characteristics: Using least square method (graphically); - EMF values in the range $0,4 - 0,6$ V; ($0,3 - 0,7$ V); - Internal resistance in the range $4,5 - 6,5$ kOhm ($4,0 - 7,0$ kOhm) The error assessment of the parameters is carried out $2 \times 0,1$	1,0	0,2(0,1) 0,3(0,2) 0,3(0,2) 0,2
Part 3. Connections of galvanic cells.		1,0	
3.1	Circuit 1: summation of EMFs; Circuit 2: subtraction of EMFs; Circuit 3: EMF of the industrial cell; Circuit 4: EMF of the industrial cell.	0,6	0,1 0,1 0,2 0,2
3.2	Theoretical formulas circuits 1-2; $0,1 \times 2 = 0,2$ circuits 3-4 (sufficient argumentation based on comparison of internal resistances); $0,1 + 0,1 = 0,2$	0,4	0,2 0,2
Part 4. Current-voltage characteristic of a galvanic cell. Graded if the results differ from the author's by no more than 50%!		13	
4.1	- measurements are carried out with two polarities of the source connection; - two branches with opposite signs of currents and voltages are obtained;	3,0	0,2 0,4

	- each branch has 8 or more points (5-7); - the range of current change on each branch is not less than 50 μA; - at negative currents a linear dependence is obtained; - at positive currents, the dependence is nonlinear, with a convexity downwards; Graph (as in part 1.3).		2x0,4(0,2) 2x0,3 0,2 0,4 0,4
4.2	Two linear sections have been allocated: one on one branch, the second on the other; 2x0,5=1,0 The values of EMFs and internal resistances are found for each section (allowable error – 50%) 0,5x4=2,0	3	1,0 2,0
4.3	- measurements are carried out with two polarities of source connection; - two branches with opposite signs of currents and voltages are obtained; - the current strength ranges overlap; - each branch has 8 or more points (5-7); - the range of current change on each branch is not less than 70 μA; - values obtained are close ($\pm 20\%$) to the values of part 4.1 in the same ranges of current strengths; - a transition from one branch to another is obtained; - zero crossing in the range of 30 – 80 μA; graph (as in part 1.3):	3,5	0,2 0,4 0,2 2x0,4(0,2) 2x0,3 2x0,2 0,3 0,2 0,4
4.3	3 linear sections have been detected; Smoothing lines are drawn; The values of EMF and internal resistance are found for each linear section; - when the sign of the current strength changes, the internal resistance changes by more than 1.5 times; - the sign of the EMF changes during polarization reversal.	3,5	3x0,3 3x0,1 6x0,3 0,2 0,3
	TOTAL	20,0	